 


Evaluating Interconnection Networks for Exposed Datapath Architectures

Motivation: SCAD-Machines

- **Synchronous Controlflow**
Asynchronous Dataflow
- Processing Units with Buffers
 - Operate as soon as inputs are available
- Move instructions move data between buffers
 - Data Transport Network
 - Interconnect N PUs with N PUs




Interconnection Networks

- Classic approaches:
 - Buses
 - Only one move at a time
 - Multiple parallel buses may not scale well
 - Crossbar Switches
 - Matrix with $N \times N$ switches
 - Allows to route N pieces of data from N source to N destinations in parallel
 - Needs global configurations for switches
- Better: Interconnection Networks



Sorting Networks

 - Structure
 - Compare and Swap units
 - Switches with attached control logic
 - Interconnected by wires
- Transport/Sort all inputs in parallel
- Routing decisions are local
- Interconnection Networks
 - Transport Address-Data-Tuples
 - Sort by address



Koppelman-Oruç Network

  - Computes ranks of input addresses
 - Prefix sum over address MSBs
 - Uses tree of adders
- Routed using Cube Network
 - Switch position based on rank LSB and address MSBs
$$p = (a_u \wedge \neg r_l) \vee (\neg a_u \wedge r_u)$$
 - Rank LSBs are dropped after each column
 - Address MSBs are dropped on recursion





Narasimha's network

- Routing based on the address MSBs and a „carry“

$$p = c_i \oplus a_u \quad c_{i+1} = (a_u \oplus a_l) \oplus c_i$$

  - Carry spans the entire first column of the network
- Address MSBs are dropped before recursion




Intel HARP

- Hardware Accelerator Research Project
- Xeon CPU with FPGA based accelerator
- hardware platform and software framework
- Primarily aimed at Datacenter applications
- FPGA and CPU share the same Memory
 - Low latency data exchange
- Programmable in VHDL OpenCL

OpenCL

- Programming language and runtime environment
- Based on the C language and C99 standard
 - Removes: Recursive functions, pointer arithmetic, dynamic memory management
 - Adds: vector operations and vector datatypes
 - Memory segmented in regions
- Runs Kernels on Compute Units attached to a host system
- Multiple kernels can be run in parallel

Intel HARP and OpenCL

 


Network Generator

- Translates hardware circuits for networks into OpenCL
 - Complete network in a single Kernel
 - Using vector operations for parallelism
 - Limited to 16 inputs by OpenCL vector types
- Four stages:
 - Leveled circuit
 - Integer circuit
 - Vector operations
 - OpenCL codes

Leveled Circuits

 - Netlist format: gates connected by wires
- Split into levels of gates
 - No data dependencies within levels
- Mostly bit-wise operations
- Data and addresses routed in the same bitvector



Leveled Circuits: Gates

Type	Inputs	Output	Operation
NOT	x	$[\neg x]$	Boolean negation
AND	x, y	$[x \wedge y]$	Boolean conjunction
OR	x, y	$[x \vee y]$	Boolean disjunction
XOR	x, y	$[x \oplus y]$	Exclusive disjunction
HA	x, y	$[x \oplus y, x \wedge y]$	Half adder
FA	x, y, z	$[x \oplus y \oplus z, x \wedge y \vee z \wedge (x \oplus y)]$	Full adder
PG	g_1, p_2, g_2, p_2	$[p_1 \wedge p_2, g_2 \vee (p_2 \wedge g_1)]$	Propagate-generate gate
MX	$c, [x_0, x_1, \dots x_n], [y_0, y_1, \dots y_n]$	$[c?y_0:x_0, c?y_1:x_1, \dots c?y_n:x_n]$	2:1 multiplexer
SW	$c, [x_0, x_1, \dots x_n], [y_0, y_1, \dots y_n]$	$[c?y_0:x_0, c?y_1:x_1, \dots c?y_n:x_n, c?y_0:x_0, \dots c?y_n:x_n]$	Switch gate

Integer Circuits

- Basic datatype in OpenCL is an integer
 - Bitvectors need to be translated to integers
 - Single wires need to become integers as well
- Splits Switches into separate address and data switches
 - Simplifies code generation later
- Introduces SubSig gates in new levels
 - Needed to extract single bits from bitvectors/integers
- Replaces ranking tree with special gate
- Reschedules resulting circuit in new levels

Vector Operations

- Use vector operations to exploit parallelism in the circuit
- Main Goal:
Merge switches of one level into shuffle instruction
- Secondary Goal:
Vectorise address logic if possible
- Levels of the circuit already group gates suitable for vectorising
- Turn the circuit into a stream of vector operations

Vector Operations

Type	Inputs	Output	Operation
NOT	x	$\neg x$	Boolean negation
AND	x, y	$x \wedge y$	Boolean conjunction
OR	x, y	$x \vee y$	Boolean disjunction
XOR	x, y	$x \oplus y$	Exclusive disjunction
MX	c, x, y	$c?y:x$	2:1 Multiplexer
SW	c, x, y	$c?y:x, c?y:y$	Switch gate
SUBSIG	x	y with $y \subseteq x$	Extract the bits in y from x
RANKINGTREE	$x_0, x_1 \dots x_n$	$r_0, r_1, \dots r_n$	Compute ranks of inputs

Vectorisation Strategy

- Start with vectors for addresses and data
- Vectorise gates of the same type in the same level if:
 - All elements of a vector are inputs of the same type of gate
 - Ignore the control input for switches
 - Ranking tree gates are already vectorised
- Derive output vectors

OpenCL: Logic and Arithmetic

- Direct translation
- Problem: Different values for true then scalar operators
- Only relevant for arithmetic operations

```
1 int4 x = (int4)(0,0,1,1);
2 int4 y = (int4)(0,1,0,1);
3
4 // z1 = NOT(x)
5 int4 z1 = !x;           // (-1,-1,0,0)
6 // z2 = AND(x,y)
7 int4 z2 = x && y;     // (0,0,0,-1)
8 // z3 = OR(x,y)
9 int4 z3 = x || y;      // (0,-1,-1,-1)
10 // z4 = XOR(x,y)
11 int4 z4 = x ^^ y;     // (0,-1,-1,0)
```

OpenCL: Extracting Bits


```
1 int sub_0 = (((addr_in[0] & (1 << 2)) >> 2) << 0);  
2  
3 int4 sub_4 = (((v_4 & (1 << 1)) >> 1) << 0)  
4           | (((v_4 & (1 << 2)) >> 2) << 1);
```

- Mask out the relevant bits
- Shift to right to LSB then to left to target position
- Use bitwise or to construct new integer

OpenCL: Mux

```
1 // z = MUX(c, x, y)
2 int4 z;
3 if(c) {
4     z = y;
5 }
6 else {
7     z = x;
8 }
```

OpenCL: RankingTree

 

```
1 //--- start ranking tree ---
2 int8 rank0 = (int8) (sig_1, sig_3, sig_5, sig_7,
3                      sig_9, sig_11, sig_13, sig_15);
4 rank0 = rank0 + (int8) (-1, 0, 0, 0, 0, 0, 0, 0);
5 int8 rank0_add_0 = (int8) (0, rank0[0], 0, rank0[2],
6                           0, rank0[4], 0, rank0[6]);
7 int8 rank0_0 = rank0 + rank0_add_0;
8 int8 rank0_add_1 = (int8) (0, 0, 0, rank0_0[1],
9                           0, 0, 0, rank0_0[5]);
10 int8 rank0_1 = rank0_0 + rank0_add_1;
11 int8 rank0_add_2 = (int8) (0, 0, 0, 0,
12                           0, 0, 0, rank0_1[3]);
13
14 int8 rank0_2 = rank0_1 + rank0_add_2;
15 int8 vec_24_add_1 = (int8) (0, 0, 0, 0,
16                           0, rank0_2[3], 0, 0);
17 int8 vec_24_1 = rank0_2 + vec_24_add_1;
18 int8 vec_24_add_0 = (int8) (0, 0, vec_24_1[1], 0,
19                           vec_24_1[3], 0, vec_24_1[5], 0);
20 int8 vec_24 = vec_24_1 + vec_24_add_0;
21 //--- end ranking tree ---
```

OpenCL: Switches

- Switch vector operations
 - Input vector, Control vector, Output vector
 - Element pairs in the vectors are swapped
- Shuffel instruction
 - Input vector **x**, mask vector **m**, Output vector **y**
 - $y[i] = x[m[i]]$
 - Mask has to be computed from control vector
 - Two possible values per mask element

$$\vec{m} = \vec{p}_0 + \vec{c} \cdot (\vec{p}_1 - \vec{p}_0)$$


OpenCL: Switches

```
1 //--- start switch ---
2 int8 switchCrtlVec0 = (int8)(sig_22, sig_15,
3                               sig_13, sig_0, 0, 0, 0, 0);
4 switchCrtlVec0 = switchCrtlVec0 & 1;
5 int8 shuffleInputVec0 = (int8)data_input;
6 int8 preShuffleVec0 = (int8)(0, 0, 1, 1,
7                               2, 2, 3, 3);
8 int8 shuffleCtrlVec0 = shuffle(switchCrtlVec0,
9                               convert_uint8(preShuffleVec0));
10 int8 shuffleOffsetVec0 = (int8) (6, 7, 4, 5,
11                               2, 3, 0, 1);
12 int8 shuffleCoeffVec0 = (int8) (1, -1, 1, -1,
13                               1, -1, 1, -1);
14 int8 shuffleVec0 = shuffleOffsetVec0 +
15                               shuffleCoeffVec0 * shuffleCtrlVec0;
16 int8 vec_1 = shuffle(shuffleInputVec0,
17                               convert_uint8(shuffleVec0));
18 //--- end      switch ---
```

Evaluation

- Test runs on GPU and CPU
 - Networks with 2,4,8 inputs tested exhaustively
 - Network with 16 inputs tested for evenly distributed sample
- Test in Simulations
 - Failed for more then 4 inputs
 - Likely compiler bug in shuffle

FGA Hardware Resources

 

Inputs	ALUTs		Flip Flops		RAM Cells	
	KoOr90	Nara94	KoOr90	Nara94	KoOr90	Nara94
2	3396	3304	6211	6210	44	44
4	7390	5729	8873	7147	46	46
8	21686	15020	16925	12849	50	50
16	67887	45519	38593	29119	58	58

FGA Hardware Resources: Switch

```
1 //--- start switch ---
2 int4 switchCtrlVec1 = (int4)(sig_addr_13, sig_addr_15,
3                               0, 0);
4 //                                ALUTs: 0  FFs: 0  RAMs: 0
5 int4 shuffleInputVec1 = (int4)data_input;
6 //                                ALUTs: 0  FFs: 0  RAMs: 0
7 int4 preShuffleVec1 = (int4)(0, 0, 1, 1);
8 //                                ALUTs: 0  FFs: 0  RAMs: 0
9 int4 shuffleCtrlVec1 = shuffle(switchCtrlVec1,
10                               convert_uint4(preShuffleVec1));
11 //                                ALUTs: 0  FFs: 0  RAMs: 0
12 int4 shuffleOffsetVec1 = (int4) (0, 1, 2, 3);
13 //                                ALUTs: 0  FFs: 0  RAMs: 0
14 int4 shuffleCoeffVec1 = (int4) (1, -1, 1, -1);
15 //                                ALUTs: 0  FFs: 0  RAMs: 0
16 int4 shuffleVec1 = shuffleOffsetVec1
17                               + shuffleCoeffVec1 * shuffleCtrlVec1;
18 // 32-bit Int Subtract(x2)  ALUTs: 66  FFs: 0  RAMs: 0
```

FPGA Hardware: Ranking Tree

```
1 //--- start ranking tree ---
2 int4 rankInputVec0 = (int4) (sig_addr_1, sig_addr_3,
3                             sig_addr_5, sig_addr_7);
4 //                                ALUTs: 0  FFs: 0  RAMs: 0
5 rankInputVec0 = rankInputVec0 + (int4) (-1, 0, 0, 0);
6 //                                ALUTs: 0  FFs: 0  RAMs: 0
7 int4 rankInputVec0_add_0 = (int4) (0, rankInputVec0[0],
8                                   0, rankInputVec0[2]);
9 //                                ALUTs: 0  FFs: 0  RAMs: 0
10 int4 rankInputVec0_0 = rankInputVec0 + rankInputVec0_add0;
11 // 32-bit Integer Add (x2)  ALUTs: 66  FFs: 0  RAMs: 0
12 int4 rankInputVec0_add1 = (int4) (0, 0,
13                                   0, rankInputVec0_0[1]);
14 //                                ALUTs: 0  FFs: 0  RAMs: 0
15 int4 rankInputVec0_1 = rankInputVec0_0 +
16   rankInputVec0_add1;
17 // 32-bit Integer Add (x1)  ALUTs: 33    FFs: 0  RAMs: 0
18 int4 vec_8_add0 = (int4) (0, 0, rankInputVec0_1[1], 0);
19 //                                ALUTs: 0  FFs: 0  RAMs: 0
20 int4 vec_8 = rankInputVec0_1 + vec_8_add0;
21 // 32-bit Integer Add    ALUTs: 33    FFs: 0  RAMs: 0
22 //--- end ranking tree ---
```

Future work

- Test on actual HARP hardware
- Extension to larger input sizes
- Explore different vectorisation strategies
 - Vectorize more aggressively
 - Vectorize nothing but the switches
- Test with an actual scad-machine implementation

Conclusion

- The generated OpenCL kernels work
- Vectorisation of switches into shuffle instruction is possible
- Simulation fails, due to compiler bugs
- Hardware synthesis works, but has not been tested
- Scalability might be an issue for larger inputs
- Vector operations are optimized efficiently
- Narashima's network is preferable in terms of size

Thank you for your attention